
 


ROLL NO: 20EC10043

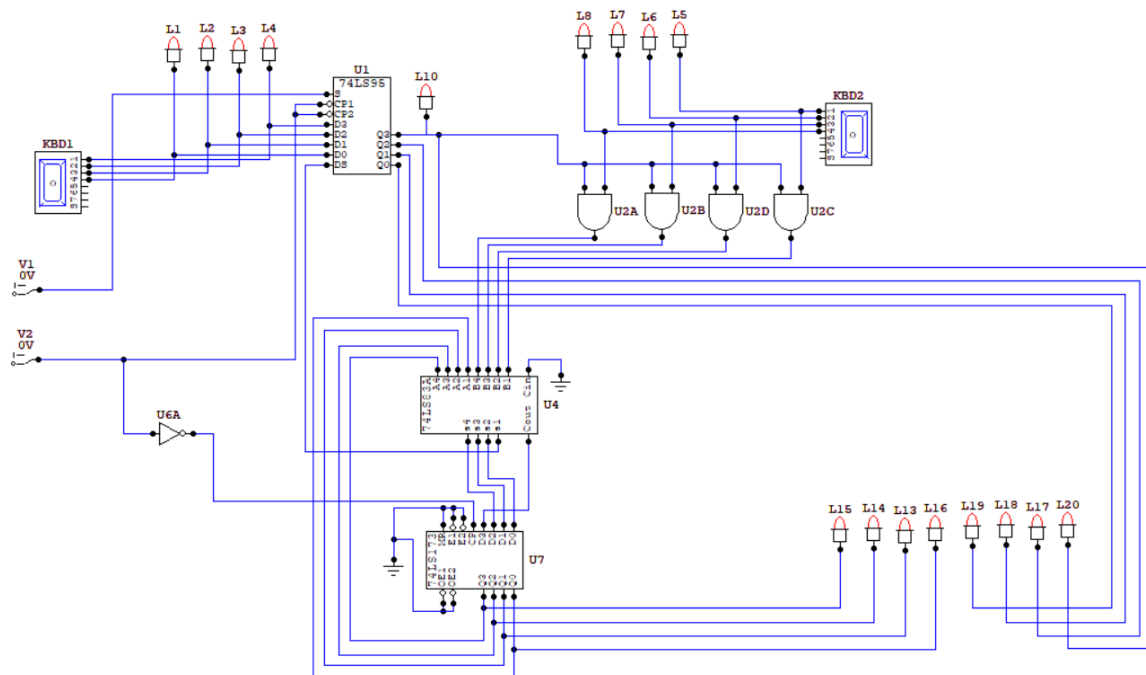

When we want to optimize the circuit, which is to reduce the circuitry involved in the experiment, we use a 4-bit register along with the shift register instead of 8-bit register and a single 4-bit full adder instead of 8-bit adder. Other than that, all others are going to remain the same.



## **BREIF THEORY AND EXPLANATION**

In this experiment, before going to the designing of the circuit, lets look at what we are trying to do. We want to create a 4x4 multiplier with the help of register and a 8-bit adder. For this, we use the concept of partial products.

$a_3 a_2 a_1 a_0$

$b_3 b_2 b_1 b_0$

-----

Final Product =  $8PP_3 + 4PP_2 + 2PP_1 + PP_0$ , where as

$PP_i = a_3 a_2 a_1 a_0 * b_i$

*So, when we multiply the multiplicand with the multiplier, we get  $PP0 + PP1(x2) + PP2(x4) + PP3(x8)$ . Here, we multiply  $x2$  for every next partial product because, when we do that, we can shift the number to left by adding a 0 at the end [ $1101(13) \rightarrow 11010(26)$ ], which is essentially what we do in normal multiplication and then add all the partial products to get the correct answer.*


*In order to get the expression like that, we use the 8-bit adder to do a different job which is to get the average of both given inputs A and B, Input B of the adder is initially 0 and then it is the result we get in the subsequent additions, A has the lower nibble to be all 0000, so that the number which is the upper nibble is multiplied by 16, which upon first addition goes to  $8PP0$ , then the number is added by  $16PP1$  and divided by 2, which results in  $8PP1 + 4PP0$ ,... and so on, we get the expected answer of  $8PP3 + 4PP2 + 2PP1 + PP0$ .*

*The circuit implementation of the first part is very much straight forward, where we use the 4-bit shift register, to shift the values of  $b_i$ , to get the respective  $PP_i$  for the addition purpose. We use the right shift property of the register to get  $b_0$  first and then  $b_1$ ,  $b_2$  and so on  $b_3$ .*

*For the second part however, we want to reduce the cost of the experiment, so we use a 4-bit register instead of 8-bit register and a single 4-bit adder in place of a 8-bit register. At the adder part, we do 4bit mean of A and B inputs of adder, which results in  $PP3/2 + PP2/4 + PP1/8 + PP0/16$ , and we give these are the upper nibble of our result. As for the lower nibble, we use the right shift register where we give the remainder of each iterative division as the serial input, which slowly gets fed as the  $Q3Q2Q1Q0$  as the 4clock pulses go, which results in our lower nibble.*

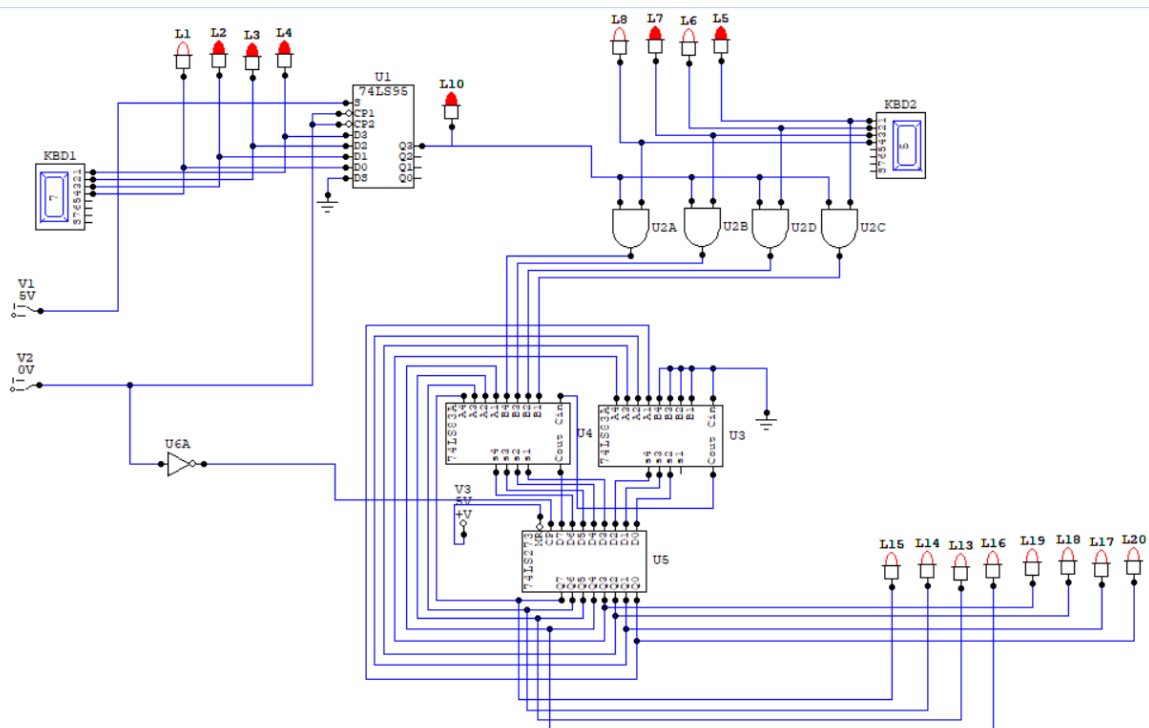
## SNAPSHOTS FROM THE EXPERIMENT



*For the first part of the experiment, we are taking the example of  $7*5=35$ .*




*S=1, and a Clock pulse to CP loads the parallel input to the output. (Parallel Loading)*

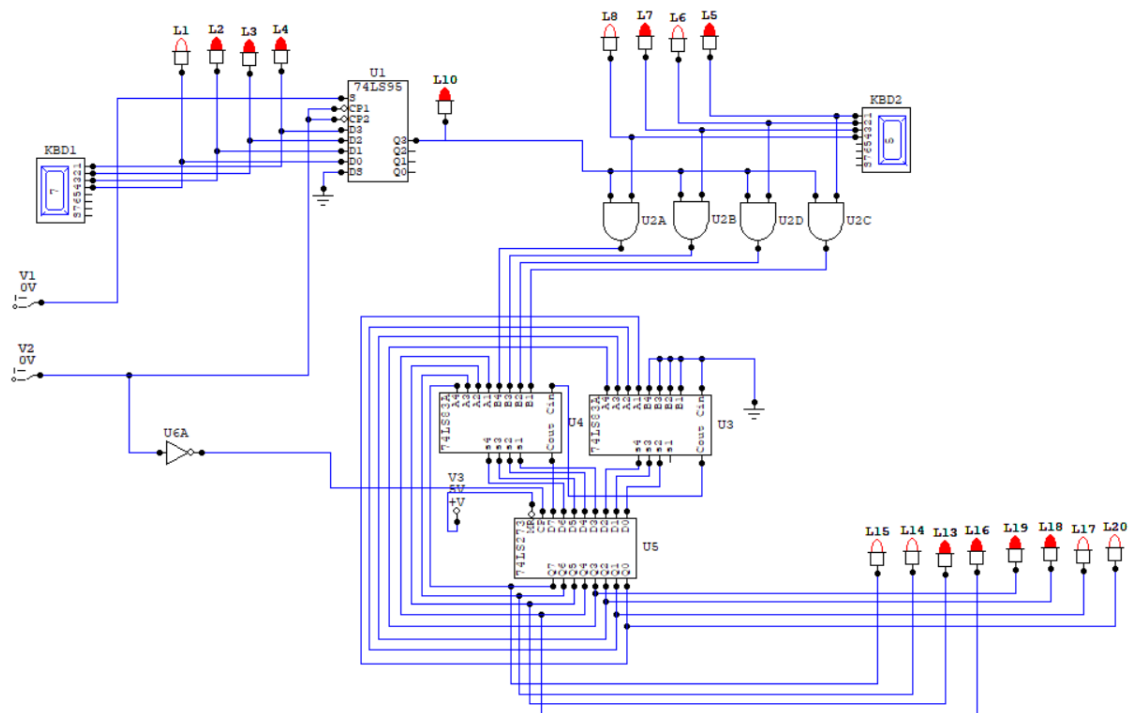*Then, we set S=0 which sets the register to right shift mode and send 4 clock pulses to do 4 iterations to get the desired result.*



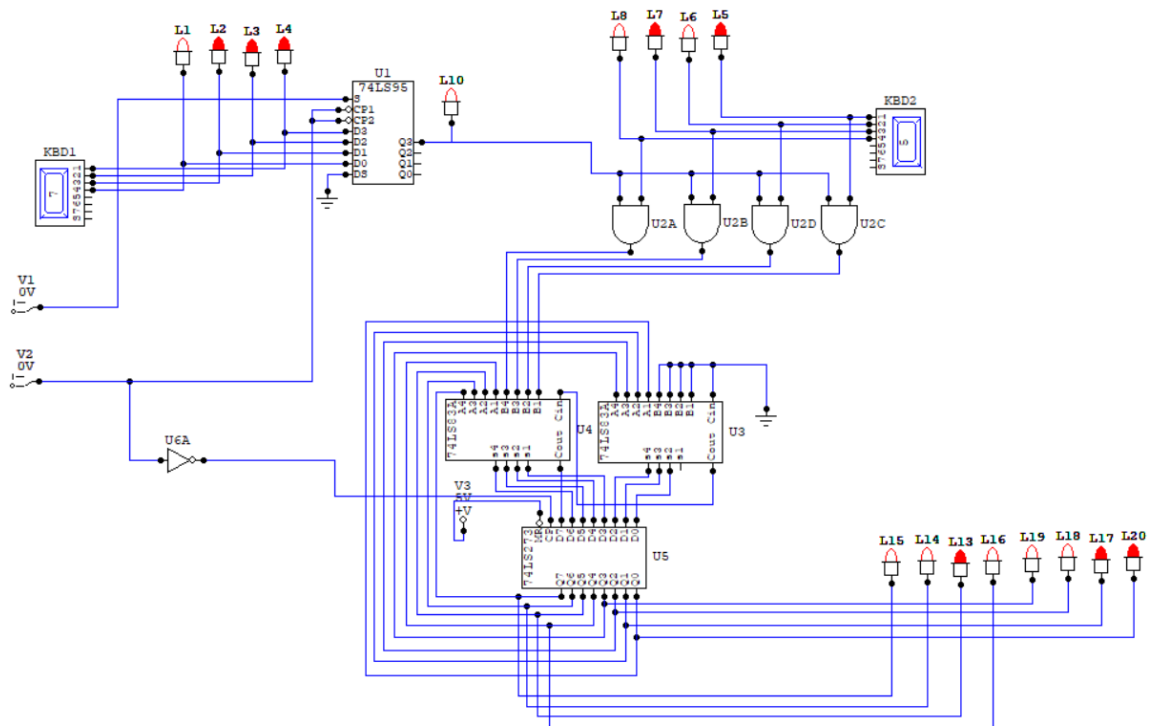
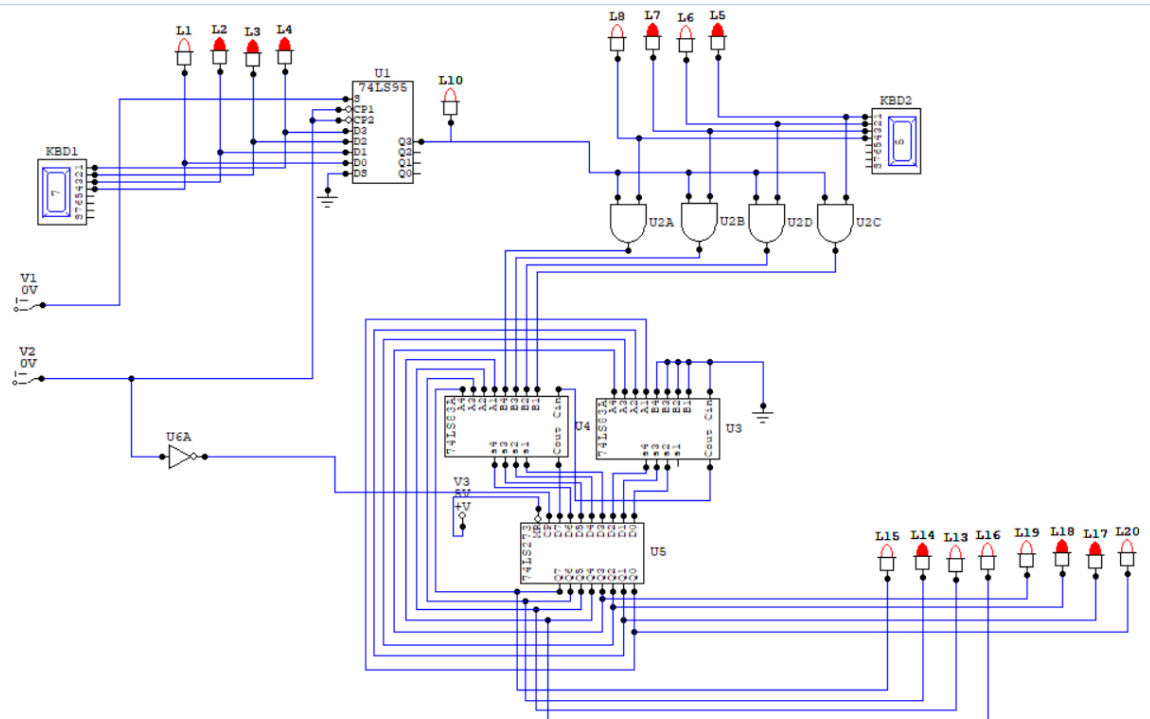


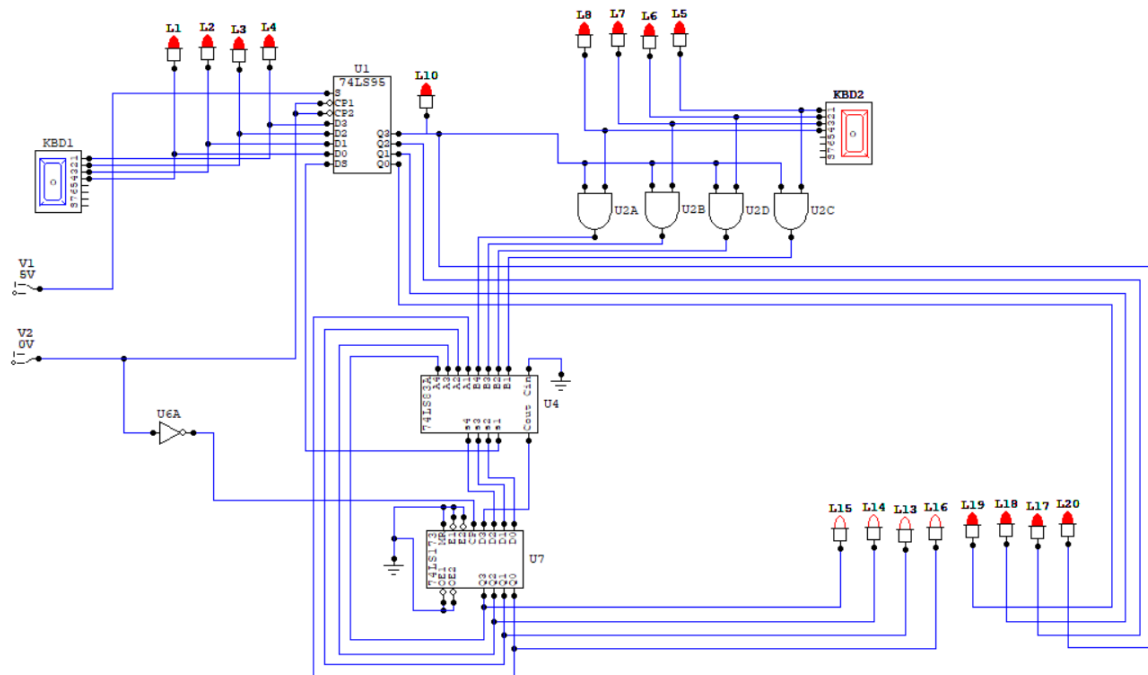For the second part of the experiment, we are taking the example of  $15 \times 15 = 225$ .




$S=1$ , and a Clock pulse to CP loads the parallel input to the output. (Parallel Loading)

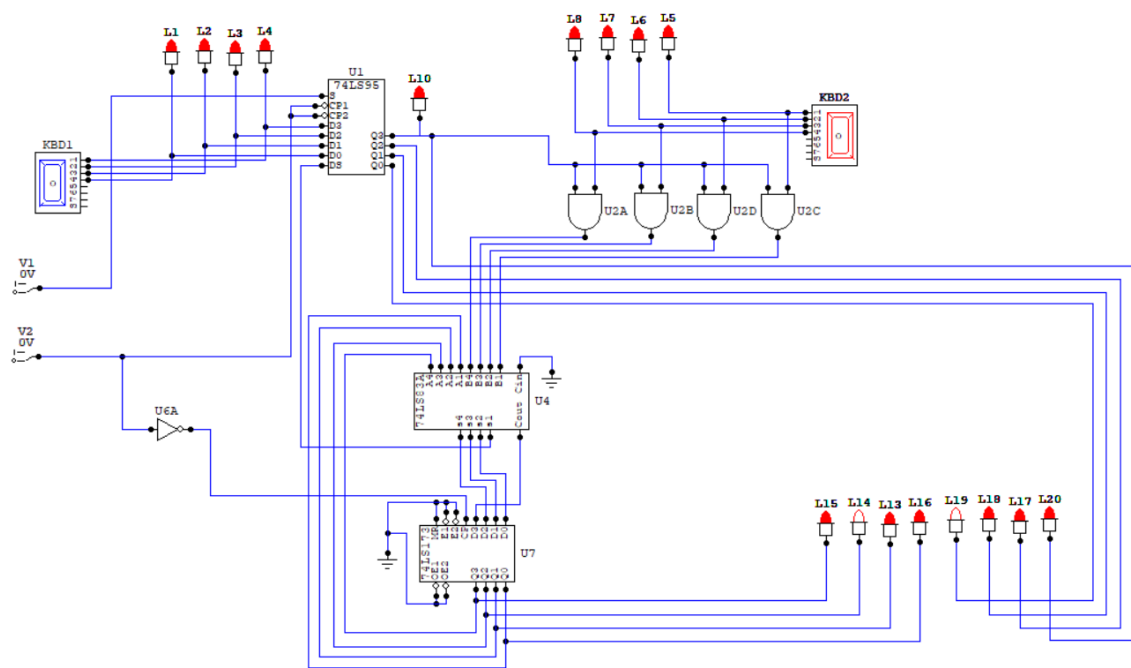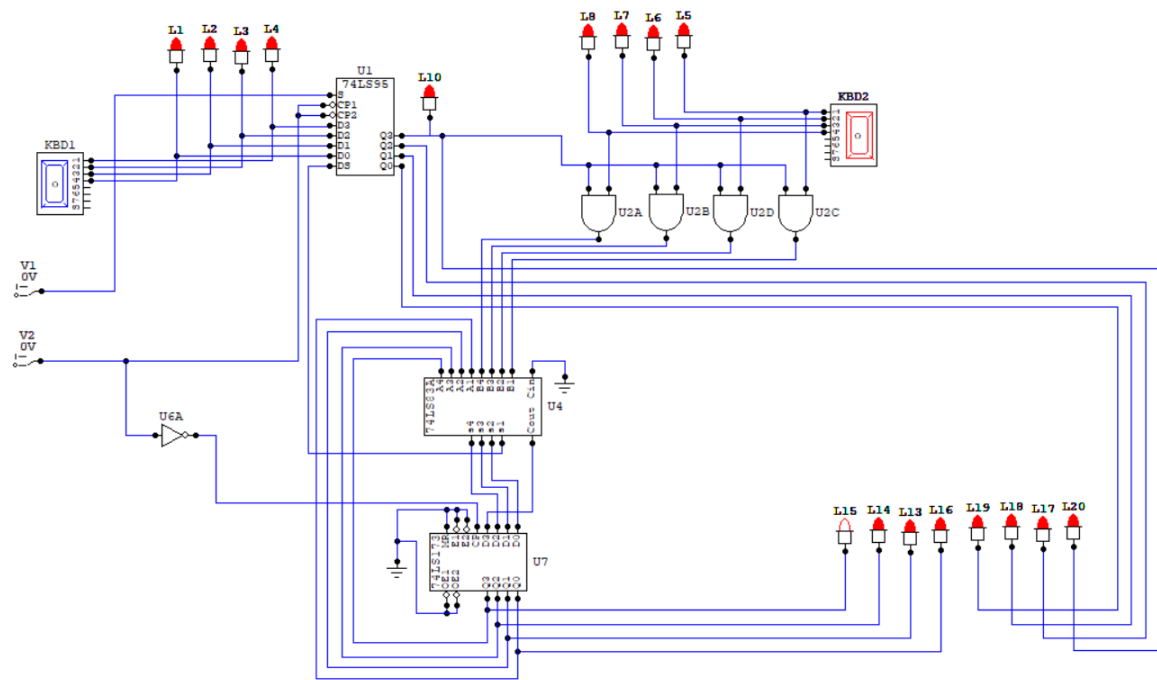Then, we set  $S=0$  which sets the register to right shift mode and send 4 clock pulses to do 4 iterations to get the desired result.





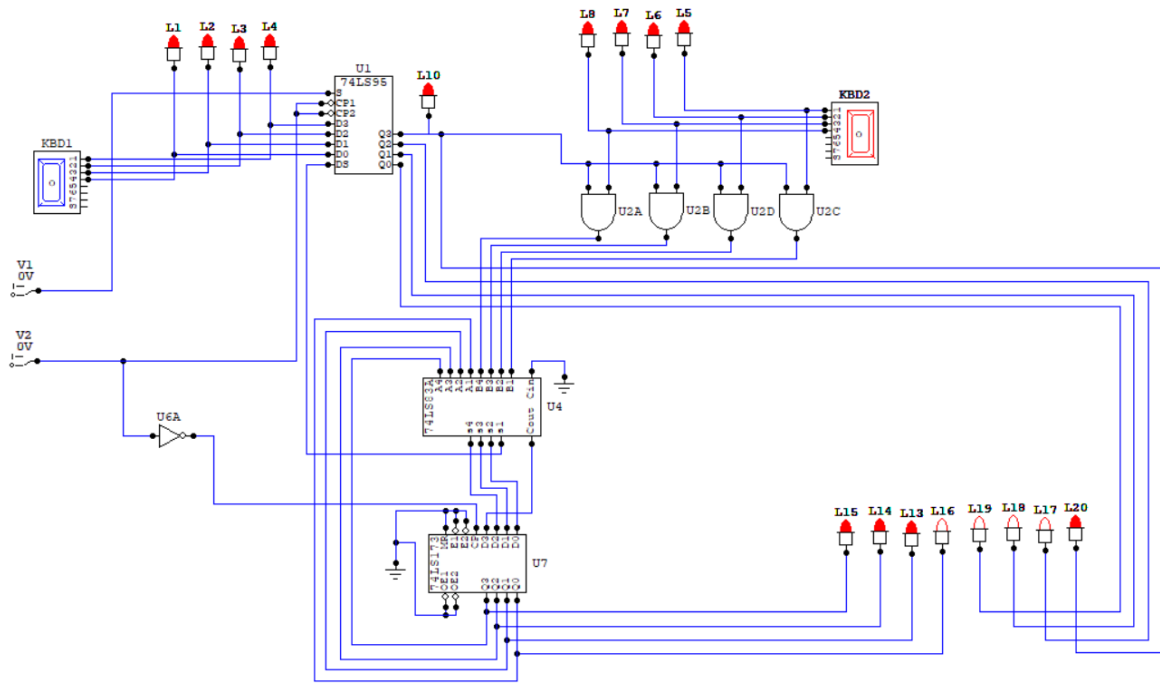

## **OBSERVATION AND CONCLUSION**

*As we see, when we check the values corresponding to the given inputs, they match accordingly, and when we try to reduce the cost by removing few circuit elements, we combine the shift register's serial input and right shift to generate the lower nibble and 4-bit adder's mean calculation as the upper nibble of our desired product.*

*For the purpose of checking, I will attach both the .ckt files along with this experiment. This takes us to the end of this experiment.*